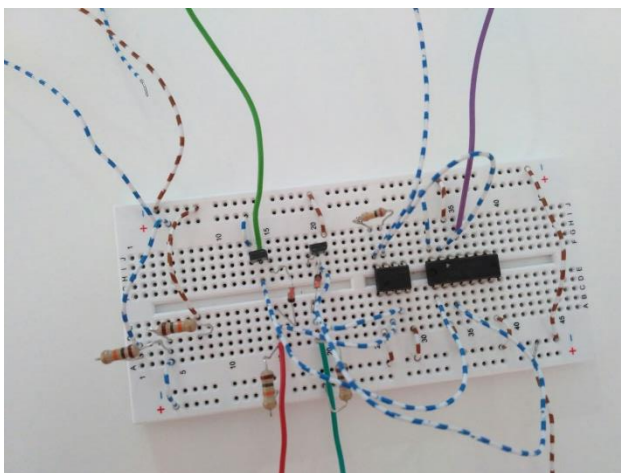


### 3. Exercise 2: CAN Transceiver Assembly

1. Provide the list of components of your transceiver and explain why you chose each of them.


- pMOSFET 1 <https://www.conrad.at/de/mosfet-diodes-incorporated-zvp2110a-1-p-kanal-700-mw-to-92-3-563632.html>
- nMOSFET 1 <https://www.conrad.at/de/mosfet-diodes-incorporated-zvnl110a-1-n-kanal-700-mw-to-92-3-563625.html>
  - PMOS and NMOS used to switch the input we receive from TX pin
- Diodes 2 <https://www.conrad.at/de/z-diode-zpd33-gehaeuseart-halbleiter-do-35-diotec-zener-spannung-33-v-leistung-max-ptot-502-mw-180041.html>
  - To transfer PMOS source output from TX to CAN\_high
  - To pass CAN\_low to NMOS drain.
- Resistors – 10k  $\Omega$ 
  - To divide voltage
- Inverter <https://www.conrad.at/de/logik-ic-gate-texas-instruments-cd4077be-xnor-exclusive-nor-4000b-pdip-14-173347.html>
  - To invert state of signal
- Comparator <https://www.conrad.at/de/linear-ic-komparator-texas-instruments-lm311p-mehrzweck-dtl-mos-offener-kollektor-offener-emitter-rtl-ttl-pdip-8-175994.html>
  - Used to get differential signal from CAN\_Low and CAN\_high

2. Provide a schematic of the circuit and highlight the driver and comparator, as in Figure 3.1.



Picture 1. Circuit


Purple wire – RX
Light green – TX
Red wire – CAN_High
Green wire – CAN_Low
Blue wire – VCC (3.3V)
Brown wire – GND
8-Dip -> Comparator
14-Dip -> NOR Inverter

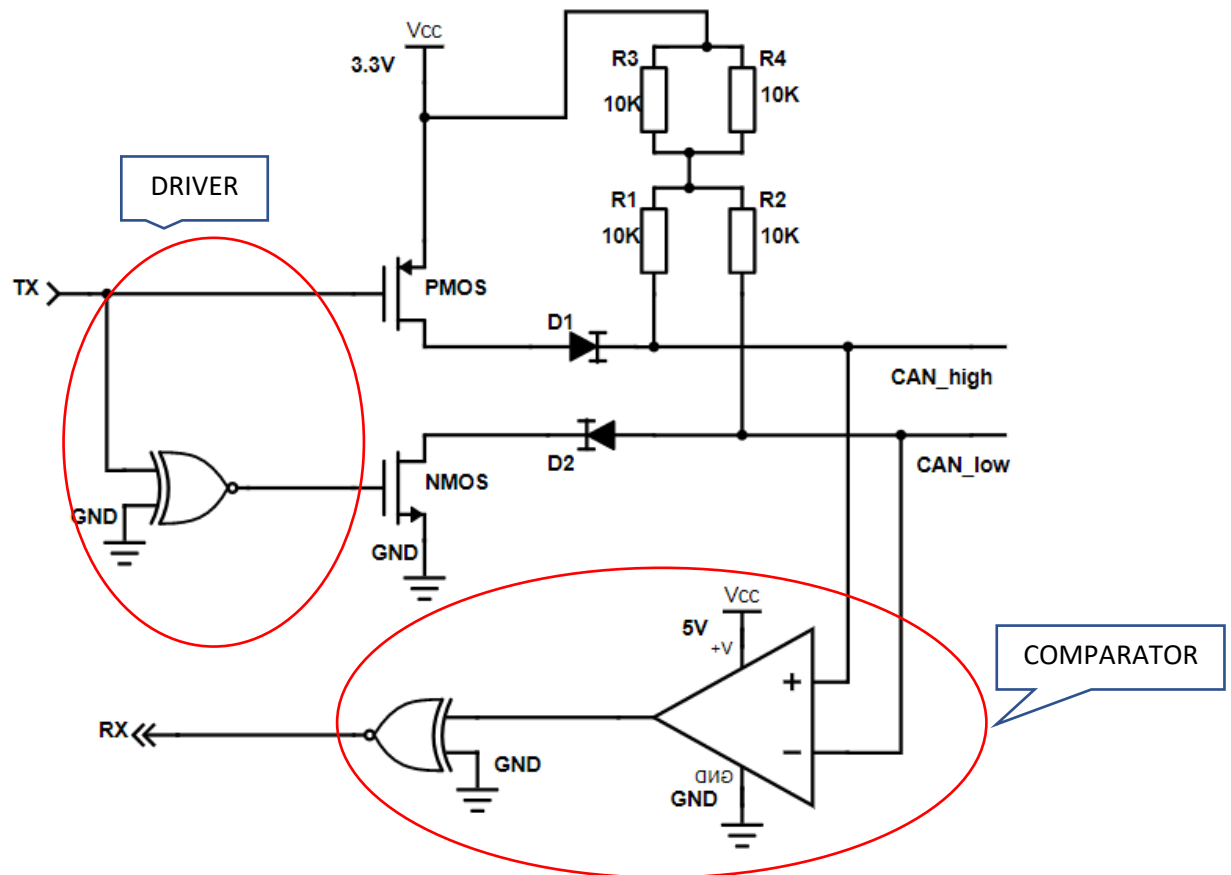


Picture 2. Schematic

3. Explain how the transceiver works and provide a screenshot showing its behavior based on the signals CANH, CANL, Tx and Rx.


- Main purpose of transceiver is to communicate between ECUs. In our case it's communication between two MSP430, with transceiver in between.
- One MSP430 at the transmitting end is connected to TX pin of transceiver and the other MSP430 is connected to RX pin at the receiving end of the transceiver.
- Whatever signal value received at TX, transceiver process the signal to the RX through different combination of components.
- If signal value of TX is 0, PMOS pass VCC to the diode and the diode transfers it to CAN\_high output. At the same time, input for NMOS is inverted and diode allows CAN\_low to pass through the NMOS transistor to ground. In our case, voltage of CAN\_low is 0.7V and CAN\_high is 2.6V.
- If TX signal value is 1, according to logic mentioned before, CAN\_low and CAN\_high gets the same value ( $VCC/2$ ). In our case, this value is 1.65 V and the state of the bus is recessive.

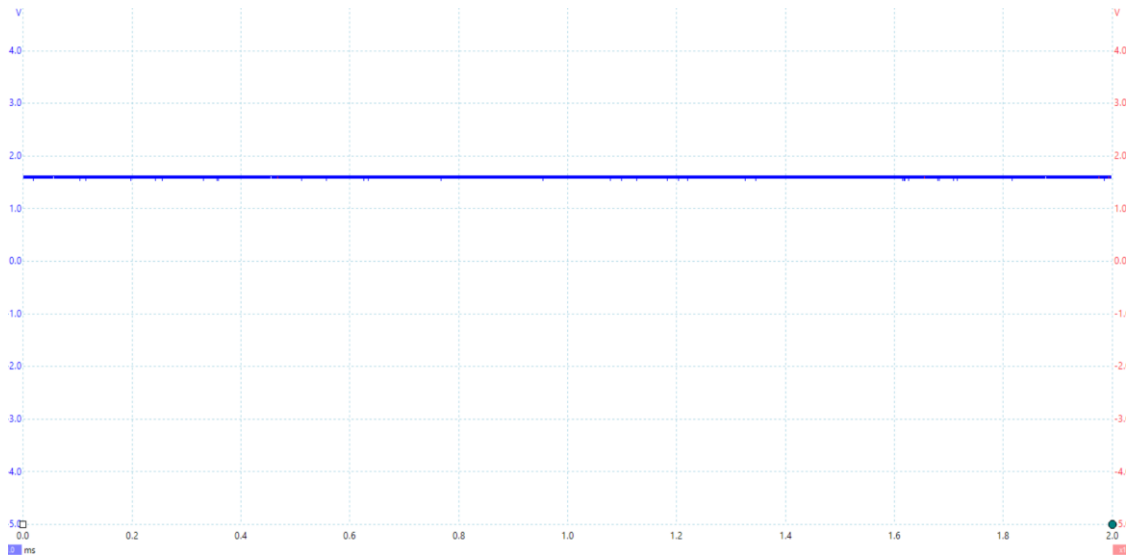

Picture 3. CAN\_low and CAN\_high - TX=1

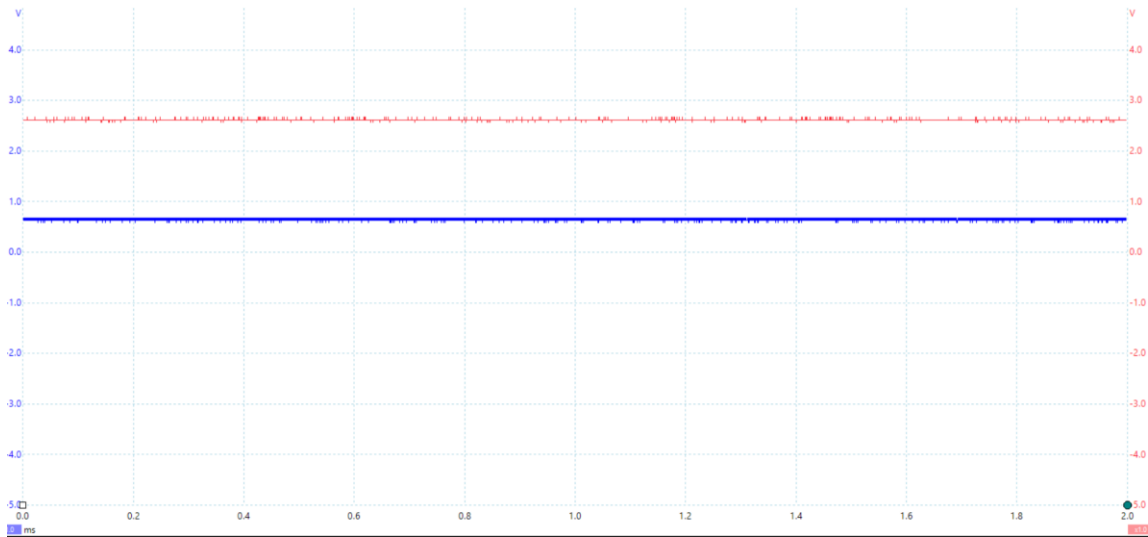


Picture 4. CAN\_low and CAN\_high TX=0

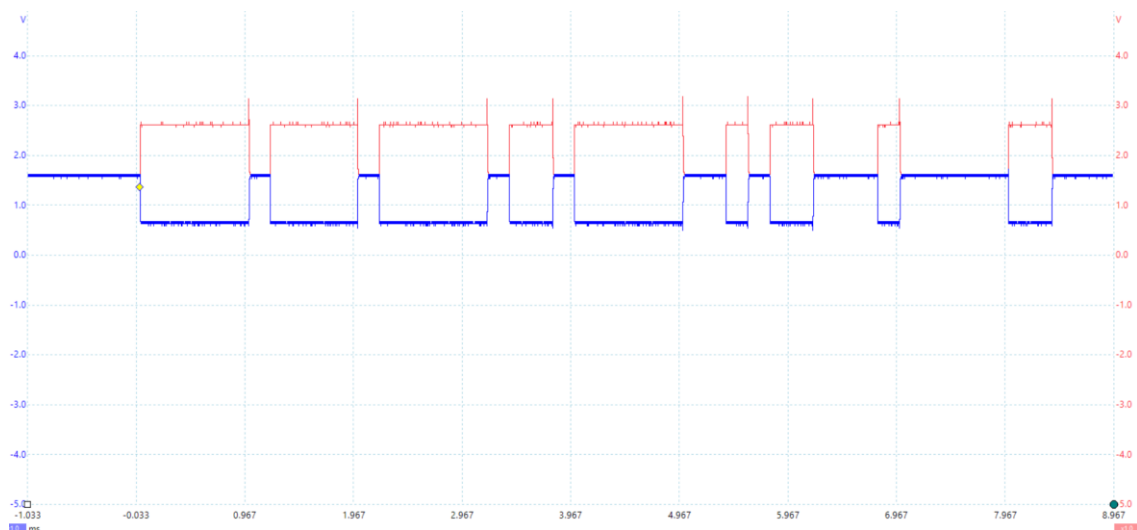

Picture 5. CAN\_low and CAN\_high - differential signal

4. Check and explain the behavior of the Rx signal in case the comparator has no hysteresis.


If comparator has no hysteresis, RX and TX would be completely synchronized. Otherwise there is small delay between RX and TX signals even for small baud rate. We can see that in picture 4.

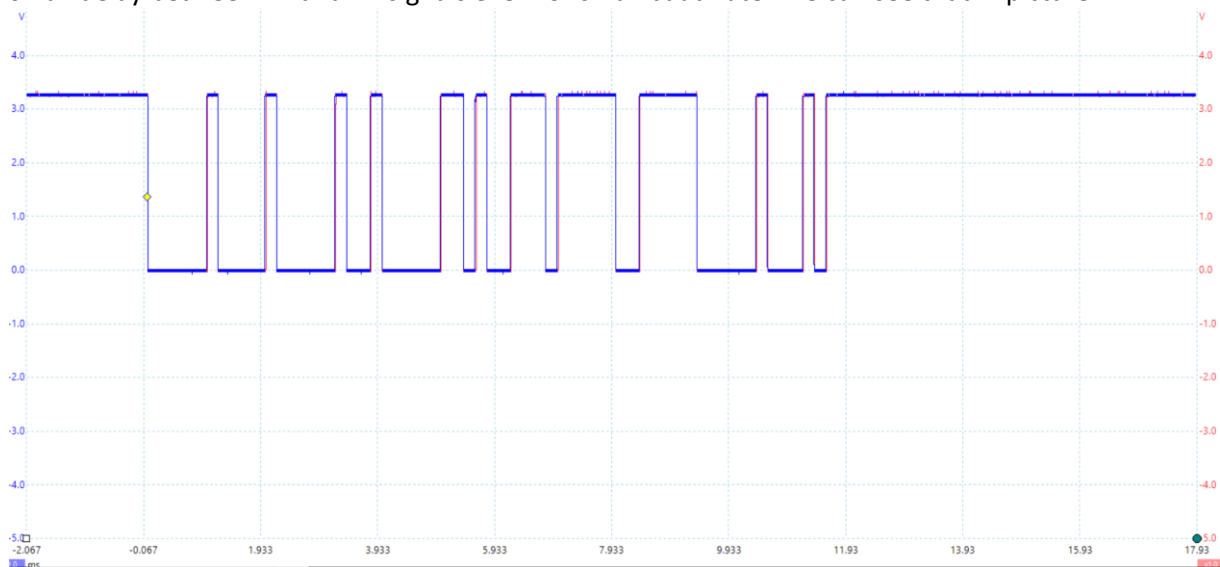

Picture 6. Baud rate 5000

5. What is the propagation time from Tx to the lines CANH and CANL? And from the lines CANH and CANL to Rx?


- As we can see in the picture below -> propagation time is 13.57 $\mu$ s

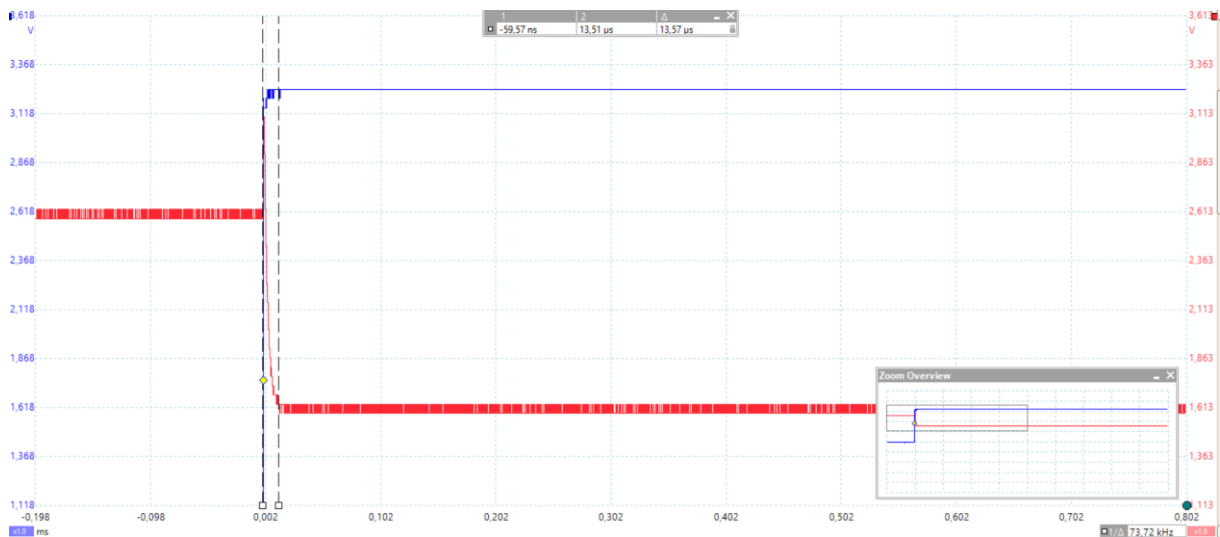


Picture 7. CAN propagation time

6. What is the transceiver's maximum supported baud rate? Explain how this value was obtained.


- Transceiver's maximum supported baud rate is 22000, everything higher than this baud rate results with RX reflects TX less than 50% of a bit width.

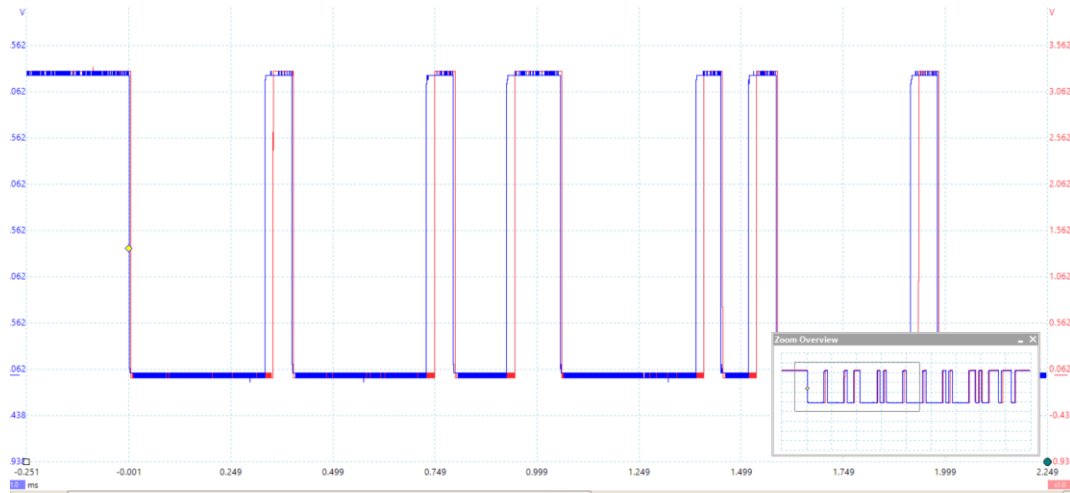

Picture 8. Baud rate 15000

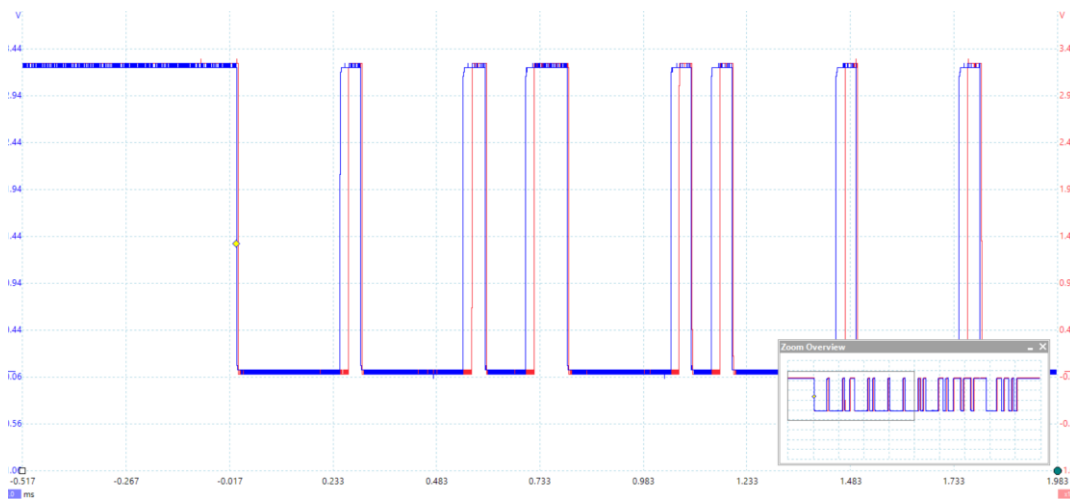

Picture 9. Baud rate 20000

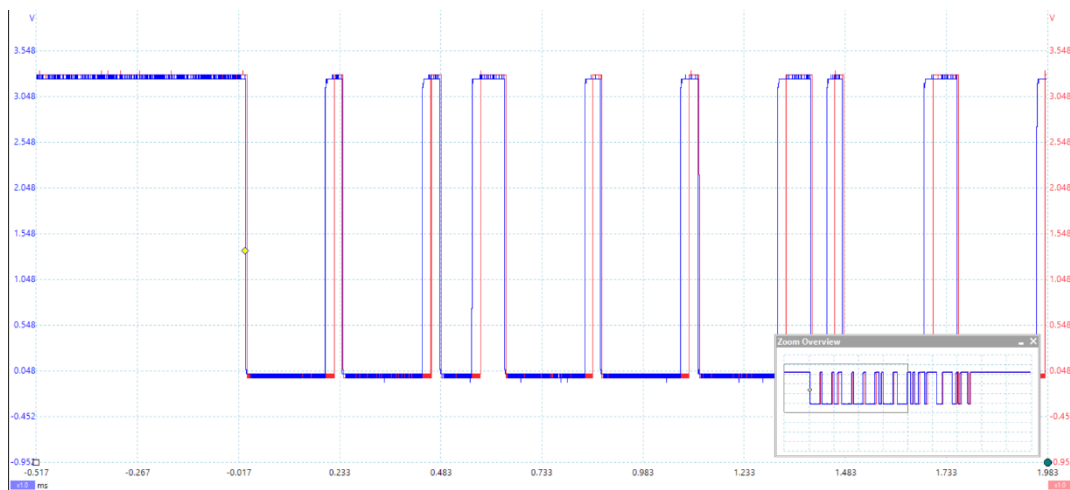

Picture 10. Baud rate 25000